

Lecture 7  
Basic gain cell  
The Common-Gate Amplifier as  
Current Buffers

---



Taha Ahmed

## 1 Basic gain cell

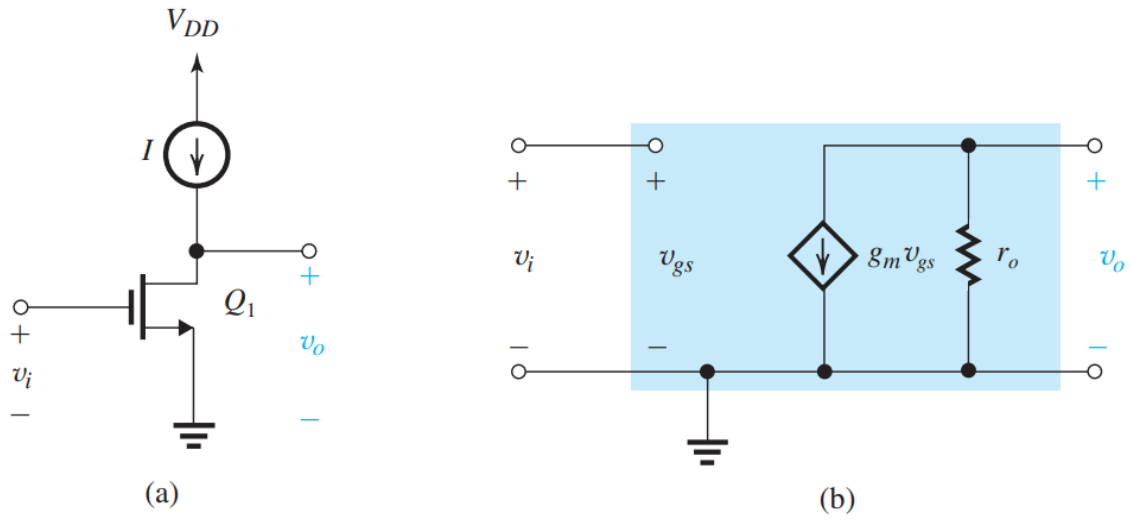


Figure 1: The basic gain cells of IC amplifiers: (a) current-source- or active-loaded common-source amplifier; (b) small-signal equivalent circuit of (a).

$$R_{in} = \infty \quad (1)$$

$$A_{vo} = -g_m r_o \quad (2)$$

$$R_o = r_o \quad (3)$$

## 2 Effect of the Output Resistance of the Current-Source Load

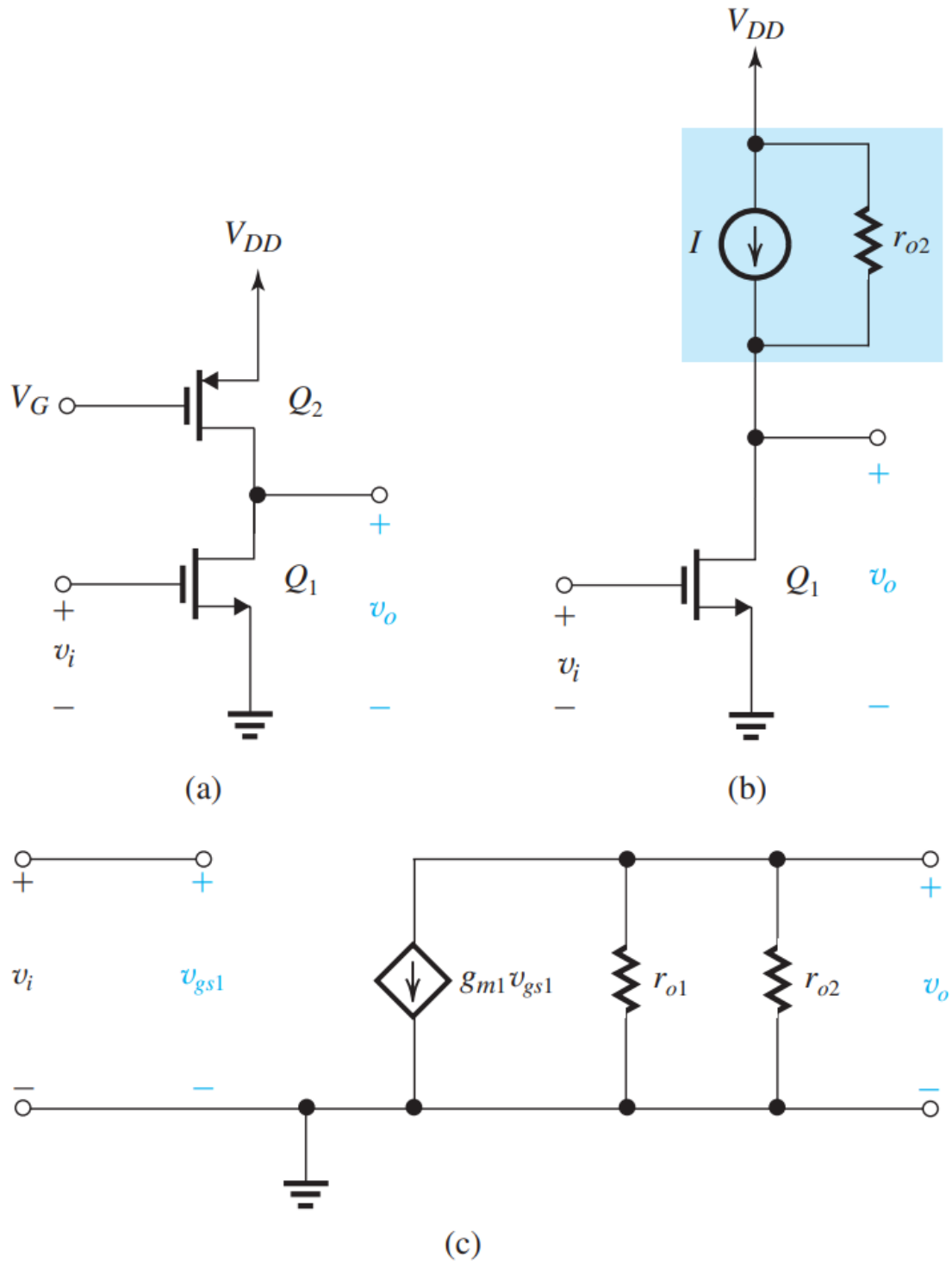



Figure 2: (a) The CS amplifier with the current-source load implemented with a *p*-channel MOSFET  $Q_2$ ; (b) the circuit with  $Q_2$  replaced with its large-signal model; and (c) small-signal equivalent circuit of the amplifier.

$$A_{vo} = -g_{m1}(r_{o1}||r_{o2}) \quad (4)$$

$$\text{If } r_{o1} = r_{o2} \quad (5)$$

$$\therefore A_{vo} = -\frac{1}{2}g_m r_o \quad (6)$$

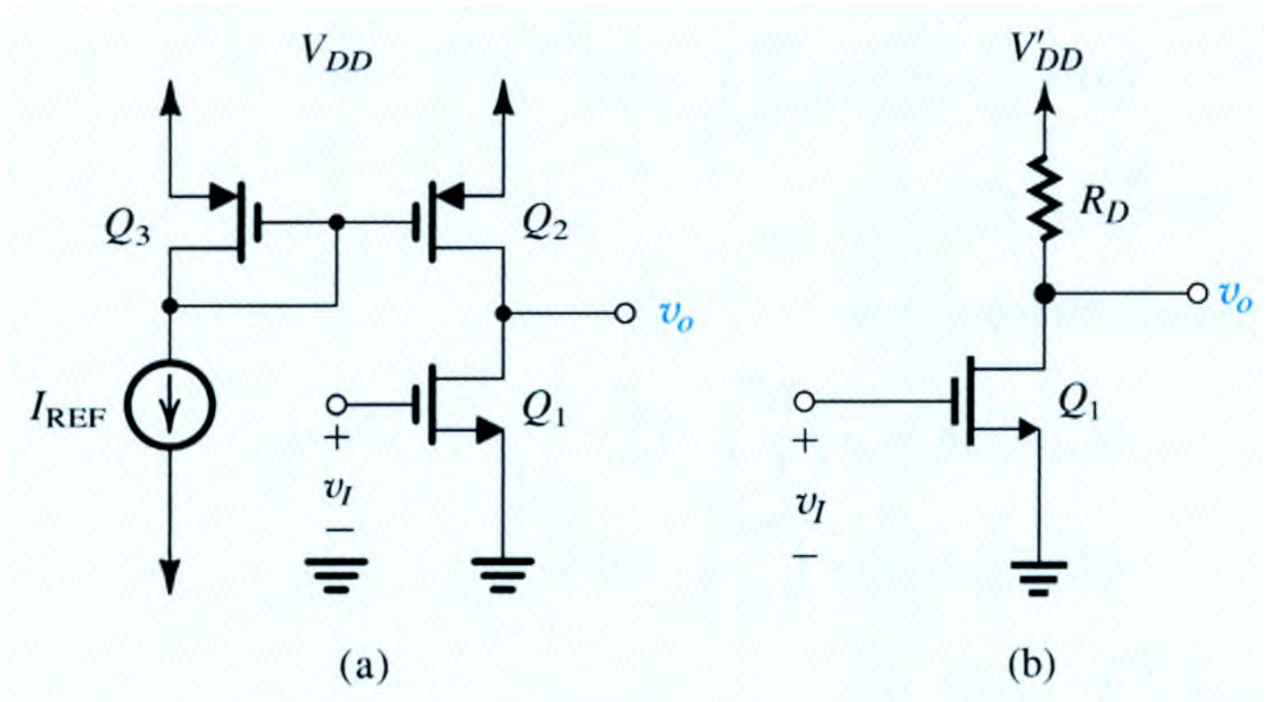**1. Q** A practical circuit implementation of the common-source amplifier with a current-source load is shown in the following figure. Here the current-source transistor  $Q_2$  is the output transistor of a current mirror formed by  $Q_2$  and  $Q_3$  and fed with a reference current  $I_{REF}$ . Assume that  $Q_2$  and  $Q_3$  are matched.



Let  $V_{DD} = 1.8 \text{ V}$ ,  $V_{tn} = -V_{tp} = 0.5 \text{ V}$ ,  $\mu_n C_{ox} = 4\mu_p C_{ox} = 400 \mu\text{A}/\text{V}^2$ ,  $|V_A| = 5 \text{ V}$  for all transistors, and  $I_{REF} = 100 \mu\text{A}$ .

(a) Find the dc component of  $v_1$ , and the  $W/L$  ratios so that all transistors operate at  $|V_{ov}| = 0.2 \text{ V}$ .

(b) Determine the small-signal voltage gain.

(c) What is the allowable range of signal swing at the output for almost-linear operation?

(d) If the current-source load is replaced with a resistance  $R_D$  connected to a power supply  $V'_{DD}$  as shown in the figure, find the value of  $R_D$  and  $V'_{DD}$  to keep  $I_D$ , the voltage gain, and the output signal swing unchanged.

**1. A**

(a) To operate  $Q_1$  and  $V_{OV} = 0.2$  V,  $V_{GS1}$  must be

$$V_{GS1} = V_{tn} + V_{OV} = 0.5 + 0.2 = 0.7 \text{ V}$$

and thus the dc component of  $v_l$  must be

$$V_I = V_{GS1} = 0.7 \text{ V}$$

Next, we determine  $(W/L)$ , from

$$I_{D1} = \frac{1}{2} (\mu_n C_{ox}) \left( \frac{W}{L} \right)_1 V_{OV}^2$$

Substituting  $I_{D1} = I_{REF} = 100 \mu\text{A}$ ,

$$\begin{aligned} 100 &= \frac{1}{2} \times 400 \times \left( \frac{W}{L} \right)_1 \times 0.2^2 \\ \Rightarrow \left( \frac{W}{L} \right)_1 &= 12.5 \end{aligned}$$

The  $W/L$  ratios for  $Q_2$  and  $Q_3$  can now be found from

$$\begin{aligned} I_{D2,3} &= \frac{1}{2} (\mu_p C_{ox}) \left( \frac{W}{L} \right)_{2,3} V_{OV}^2 \\ 100 &= \frac{1}{2} \times 100 \times \left( \frac{W}{L} \right)_{2,3} \times 0.2^2 \\ \Rightarrow \left( \frac{W}{L} \right)_{2,3} &= 50 \end{aligned}$$

(b) To obtain the small-voltage signal voltage gain, we first determine the small-signal parameters  $g_{m1}$ ,  $r_{o1}$ , and  $r_{o2}$  as follows:

$$\begin{aligned} g_{m1} &= \frac{2I_{D1}}{V_{OV1}} = \frac{2 \times 0.1 \text{ mA}}{0.2 \text{ V}} = 1 \text{ mA/V} \\ r_{o1} &= \frac{V_{A1}}{I_{D1}} = \frac{5 \text{ V}}{0.1 \text{ mA}} = 50 \text{ k}\Omega \\ r_{o2} &= \frac{|V_{A2}|}{I_{D2}} = \frac{5 \text{ V}}{0.1 \text{ mA}} = 50 \text{ k}\Omega \end{aligned}$$

The voltage gain  $A_v$  can now be found as

$$\begin{aligned} A_v &= -g_{m1} (r_{o1} \parallel r_{o2}) \\ &= -1(50 \parallel 50) \\ &= -25 \text{ V/V} \end{aligned}$$

(c) The upper limit of the output signal swing is determined by  $Q_2$  leaving the saturation region. This will occur if  $v_O$  reaches  $V_{DD} - |V_{OV2}|$ , thus

$$v_{O\max} = 1.8 - 0.2 = 1.6 \text{ V}$$

The lower limit of the output signal swing is determined by  $Q_1$  leaving the saturation region. This will occur if  $v_0$  falls below  $V_{OV1}$ , thus

$$v_{0\min} = 0.2 \text{ V}$$

Thus, the range of linear signal swing at the output is given by

$$0.2 \text{ V} \leq v_o \leq 1.6 \text{ V}$$

(d) If the current-source load is replaced with a resistance  $R_D$  as in Fig. 8.16(b), to keep the gain unchanged,

$$R_D = r_{o2} = 50\text{k}\Omega$$

To keep the output signal swing unchanged, we bias  $Q_1$  so that  $V_{DS1}$  is equal to the mid point of the output swing, that is,

$$V_{DS1} = 0.9 \text{ V}$$

Now, for  $I_D$  to be the same as before, that is,  $I_D = 0.1 \text{ mA}$ , the new supply voltage must be,

$$\begin{aligned} V'_{DD} &= V_{DS1} + I_D R_D \\ &= 0.9 + 0.1 \times 50 = 5.9 \text{ V} \end{aligned}$$

which is much larger than the supply voltage possible with this  $0.18 - \mu\text{m}$  CMOS technology (1.8 V). Needless to say, fabricating a  $50\text{k}\Omega$  resistance with precise value on the IC is an expensive endeavor. This illustrates the need for using current-source

loads.

### 3 The Common-Gate and Common-Base Amplifiers as Current Buffers

#### 3.1 The CG Circuit

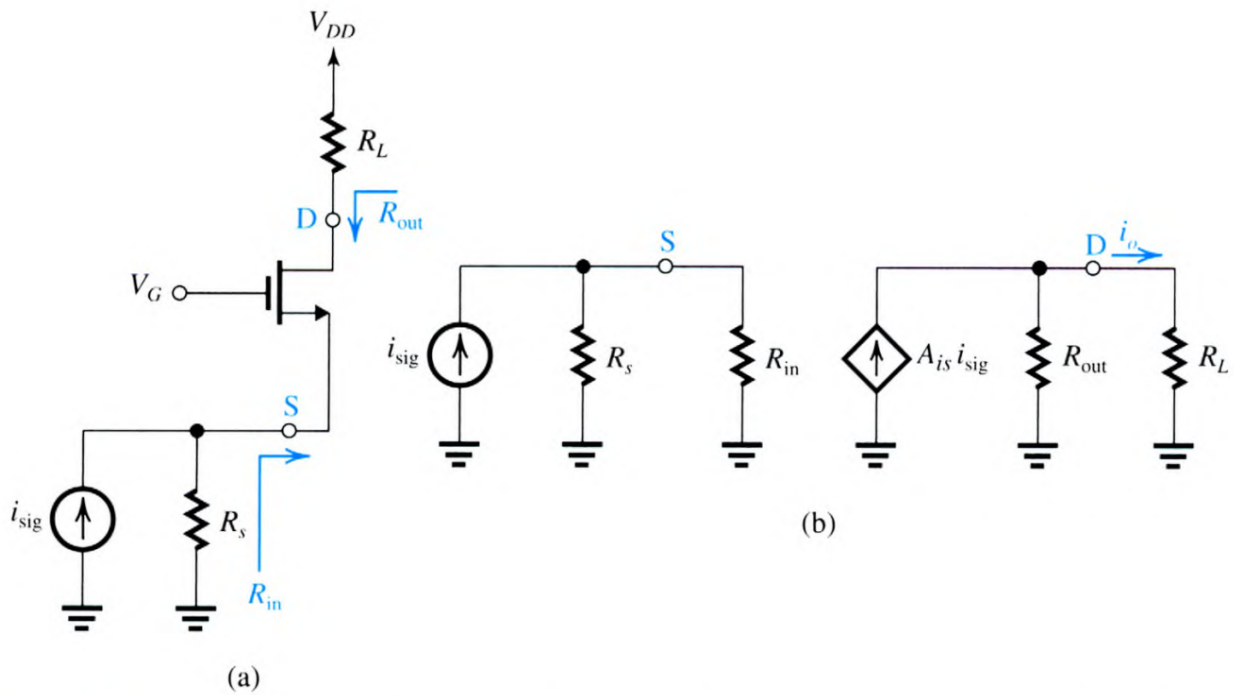


Figure 3: (a) A CG amplifier with the bias arrangement only partially shown, (b) Equivalent circuit model of the CG amplifier in (a).

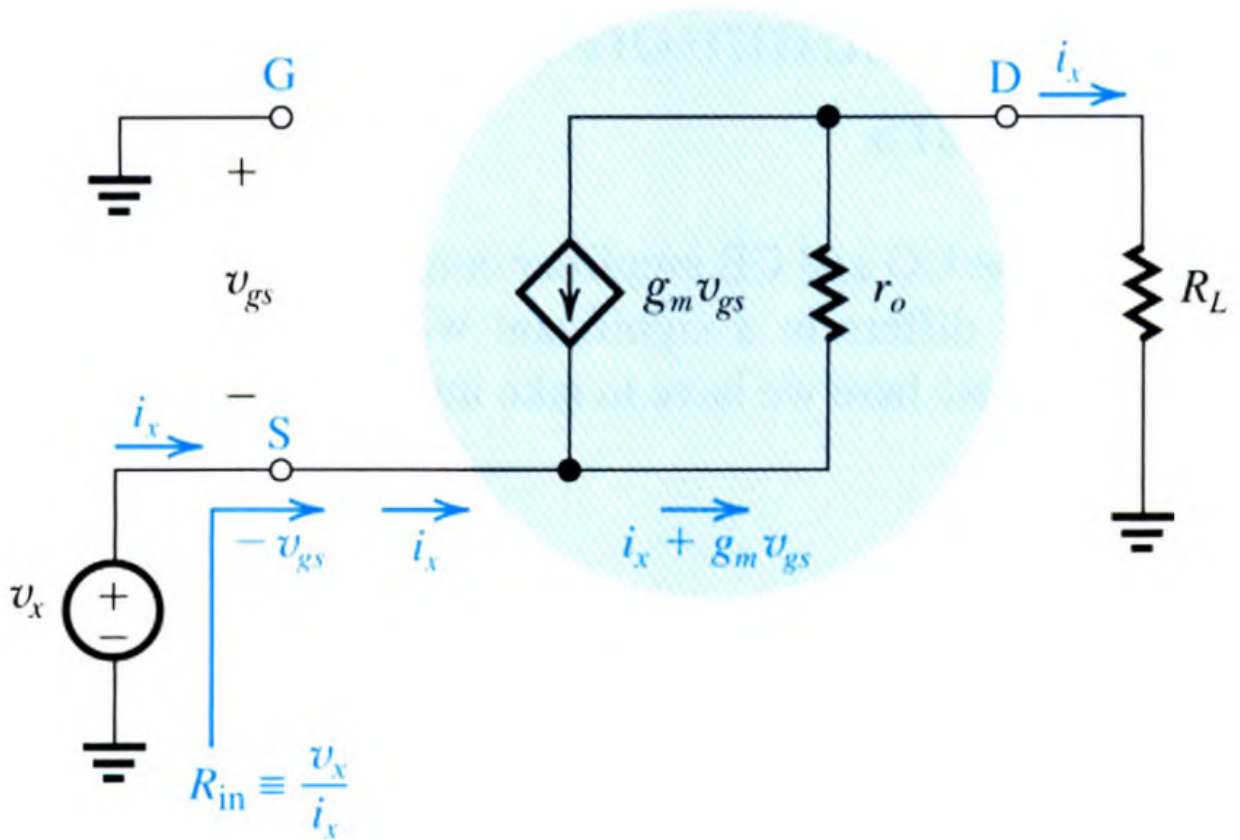


Figure 4: Determining the input resistance  $R_{in}$  of the CG amplifier.

### Input resistance :

$$R_{in} = \frac{v_s}{i_s}$$

Some of the analysis is shown in Fig. 4. Now, writing a loop equation for the loop comprising  $v_x$ ,  $r_o$ , and  $R_L$  gives

$$v_x = (i_x + g_m v_{gs}) r_o + i_x R_L$$

Since the voltage at the source node  $v_x$  is equal to  $-v_{gs}$ , we can replace  $v_{gs}$  by  $-v_x$  and rearrange terms to obtain  $R_{in} \equiv v_x / i_x$

$$R_{in} = \frac{r_o + R_L}{g_m r_o + 1}$$

For  $g_m r_o \gg 1$

$$R_{in} \simeq \frac{1}{g_m} + \frac{R_L}{g_m r_o}$$



## short circuit gain

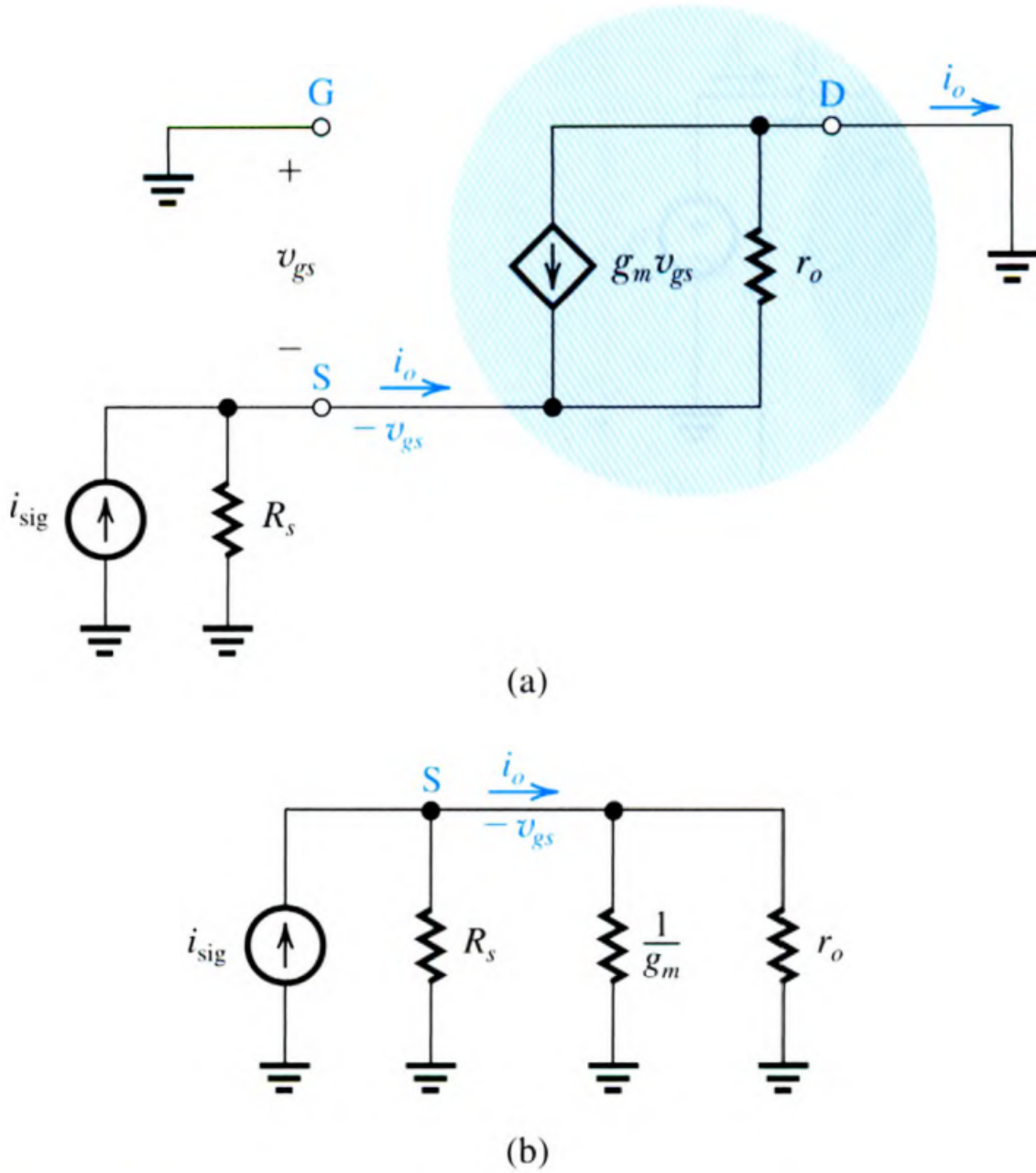


Figure 5: (a) Determining the short-circuit current gain  $A_{is} = i_o/i_{\text{sig}}$  of the CG amplifier, (b) A simplified version of the circuit in (a).

$$A_{is} \equiv \frac{i_o}{i_{\text{sig}}}$$

circuit shown in Fig. 5, from which we can find  $i_o/i_{\text{sig}}$  by using the current-divider rule:

$$A_{is} \equiv \frac{i_o}{i_{sig}} = \frac{g_m + \frac{1}{r_o}}{g_m + \frac{1}{r_o} + \frac{1}{R_s}}$$

Thus,

$$A_{is} = \frac{1 + \frac{1}{g_m r_o}}{1 + \frac{1}{g_m r_o} + \frac{1}{g_m R_s}}$$

For  $g_m r_o \gg 1$  and  $g_m R_s \gg 1$

$$A_{is} \simeq 1$$

which is an important characteristic of a current buffer.

## Output Resistance

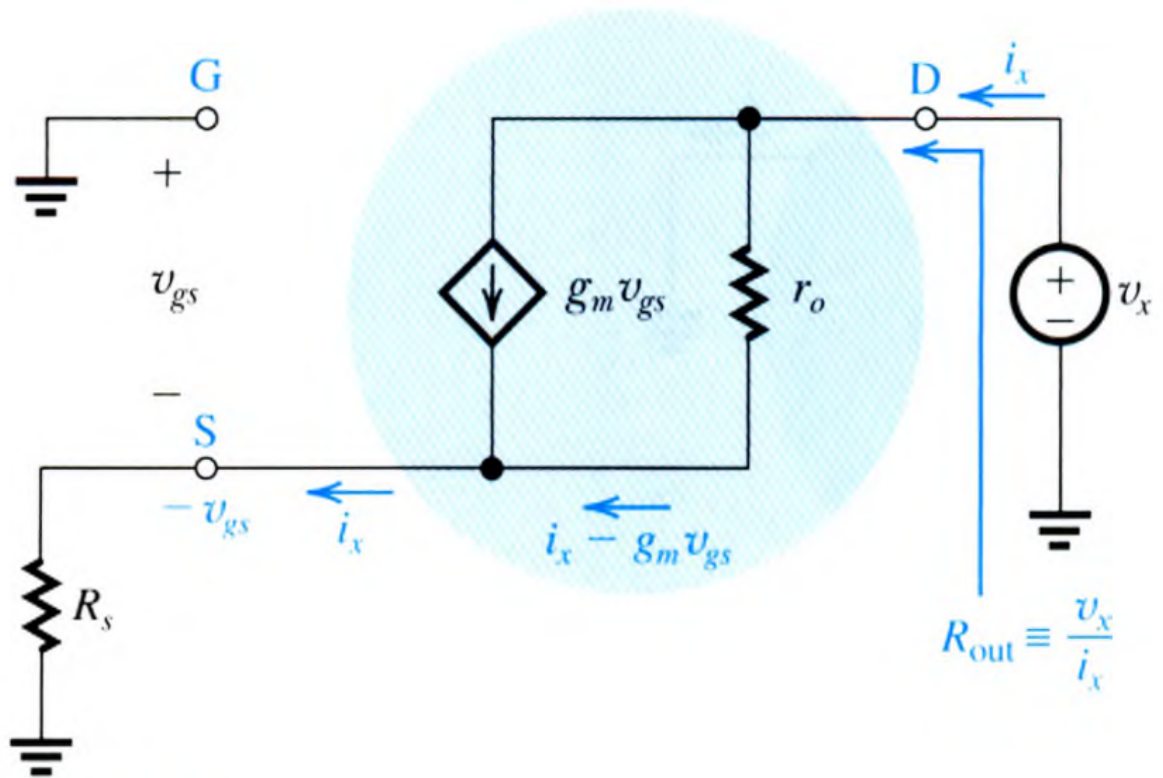


Figure 6: Determining the output resistance  $R_{out}$  of the CG amplifier.

$$R_{out} = \frac{v_x}{i_x}$$

Some of the analysis is shown in Fig. 6. Now, a loop equation for the loop comprising  $v_x$ ,  $r_o$ , and  $R_s$  gives

$$v_x = (i_x - g_m v_{gs}) r_o + i_x R_s$$

Notice that the voltage at the source terminal is  $-v_{gs}$  and thus can also be expressed as

$$-v_{gs} = i_x R_s$$

Substituting this value for  $v_{gs}$  in the previous equation and rearranging terms to obtain  $R_{\text{out}} \equiv v_x/i_x$  yields

$$R_{\text{out}} = r_o + R_s + g_m r_o R_s$$

which can be written in the alternate form

$$R_{\text{out}} = r_o + (1 + g_m r_o) R_s$$

For  $g_m r_o \gg 1$

$$R_{\text{out}} \simeq r_o + (g_m r_o) R_s$$

and if we also have  $g_m R_s \gg 1$ , then

$$R_{\text{out}} \simeq (g_m r_o) R_s$$

## Summary

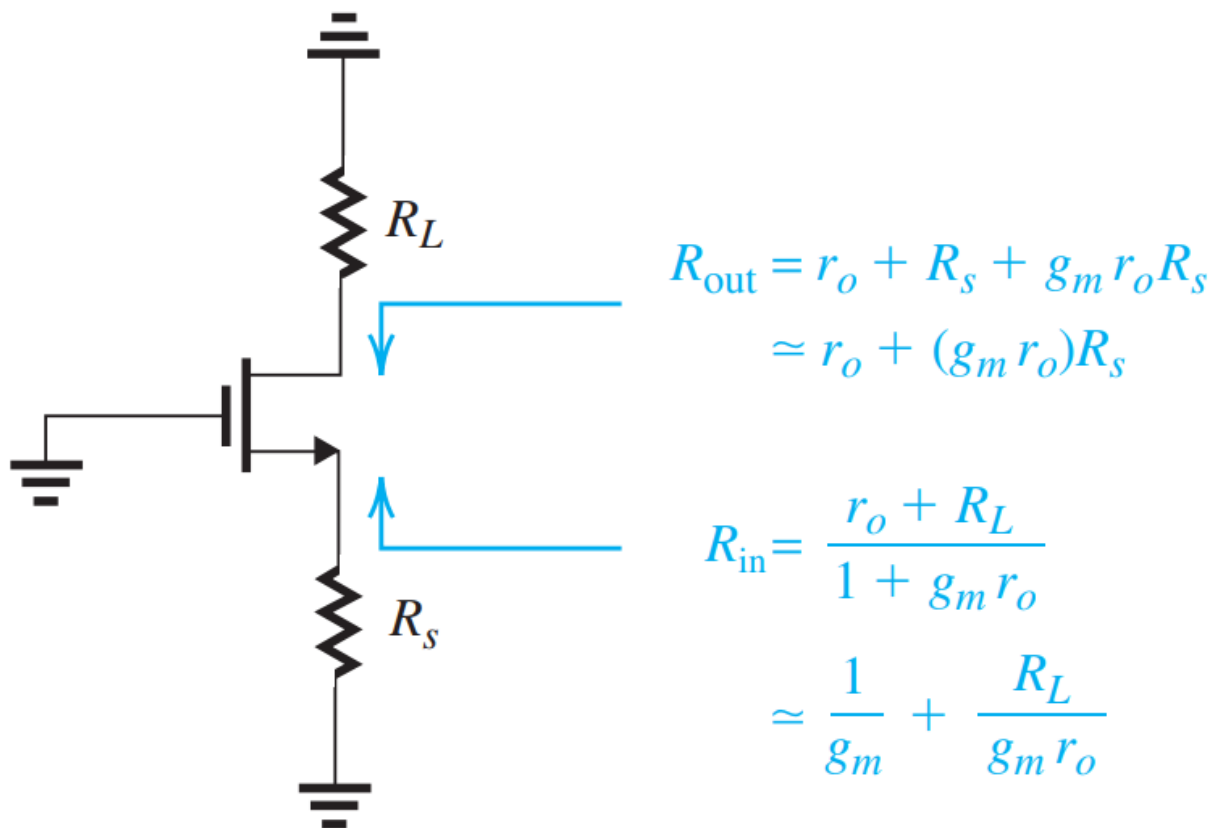


Figure 7: The impedance transformation properties of the common-gate amplifier. Depending on the values of  $R_s$  and  $R_L$ , we can sometimes write and  $R_{in} \approx R_L/(g_m r_o)$  and  $R_o \approx R_s(g_m r_o)$ . However, such approximations are not always justified