

EEC 332 - Analog Integrated Circuits

Lecture 4

MOSFET Circuits at DC



Taha Ahmed

1 The p-Channel MOSFET

To induce a channel for current flow between source and drain, a negative voltage is applied to the gate.

By increasing the magnitude of the negative v_{GS} beyond the magnitude of the threshold voltage V_{tp} , which by convention is **negative**, a p channel is established, the condition can be described as

$$v_{GS} \leq V_{tp} \quad (1)$$

therefore, v_{OV} can be calculated by

$$v_{OV} \equiv v_{GS} - V_{tp} \quad (2)$$

Saturation mode occurs when

$$v_{DS} \leq v_{OV} \quad (3)$$

1. Q Compare between n-channel MOSFET and p-channel MOSFET

1. A

	<i>n</i> -channel MOSFET	<i>p</i> -channel MOSFET
Symbol		
polarity of V_t	$V_{tn} \rightarrow$ positive	$V_{tp} \rightarrow$ negative
v_{OV}	$\underbrace{v_{OV}}_{+ve} \equiv \underbrace{v_{GS}}_{+ve} - \underbrace{V_{tp}}_{+ve}$	$\underbrace{v_{OV}}_{-ve} \equiv \underbrace{v_{GS}}_{-ve} - \underbrace{V_{tp}}_{-ve}$
In Saturation	$v_{DS} \geq v_{OV}$	$v_{DS} \leq v_{OV}$

2 MOSFET Circuits at DC

2. Q for the following circuit , find the labeled node voltages. The NMOS transistors have $V_t = 0.9 \text{ V}$ and $k'_n(W/L) = 1.5 \text{ mA/V}^2$.

2. A

For Q_2 transistor


$$\begin{aligned} i_{D2} &= \frac{V_2 - (-2.5)}{1000} \\ &= V_2 + 2.5 \text{ mA} \end{aligned} \quad (1)$$

The gate source voltage V_{GS} is $V_G - V_S$ and hence V_{GS} is equal to $(2.5 - V_1)$

The drain current for NMOS Q_1 transistor is.

$$\begin{aligned} i_{D1} &= \frac{1}{2} k'_n \left(\frac{W}{L} \right) (v_{GS} - V_t)^2 \\ &= \frac{1}{2} \left(1.5 \times 10^{-3} \frac{\text{A}}{\text{V}^2} \right) [(2.5 - V_1) - 0.9]^2 \\ &= 0.75 (1.6 - V_1)^2 \end{aligned}$$

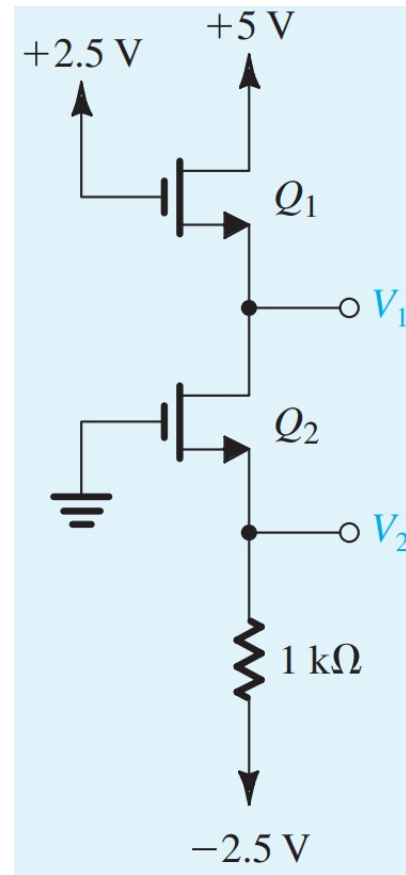Similarly, The drain current for NMOS Q_2 transistor is.



$$\begin{aligned}
i_{D2} &= \frac{1}{2} k'_n \left(\frac{W}{L} \right) (v_{\sigma s} - V_t)^2 \\
&= \frac{1}{2} \left(1.5 \times 10^{-3} \frac{\text{A}}{\text{V}^2} \right) [(0 - V_2) - 0.9]^2 \\
&= 0.75 (-0.9 - V_2)^2
\end{aligned} \tag{2}$$

$\because Q_1$ and Q_2 are in series

$$\therefore i_{D1} = i_{D2}$$

$$0.75 (-0.9 - V_2)^2 = 0.75 (1.6 - V_1)^2$$

$$-0.9 - V_2 = 1.6 - V_1$$

$$V_1 - V_2 = 2.5 \text{ V}$$

Equate (1) with (2) :

$$0.75 (-0.9 - V_2)^2 = V_2 + 2.5$$

$$0.75 (0.81 + V_2^2 + 1.8V_2) = V_2 + 2.5$$

$$0.6075 + 0.75V_2^2 + 1.35V_2 - V_2 - 2.5 = 0$$

$$0.75V_2^2 + 0.35V_2 - 1.8925 = 0$$

Solve the quadratic equation

$$\therefore V_2 = -1.877 \quad \text{or} \quad V_2 = 1.37 \text{ V (rejected)}$$

We rejected the positive value because v_{GS} should be greater than V_t for the MOSFET to operate

Thus, the voltage V_2 is -1.877 V

From the equation $V_1 - V_2 = 2.5 \text{ V}$

$$V_1 - V_2 = 2.5 \text{ V}$$

$$V_1 = 2.5 - 1.877$$

$$V_1 = 0.623 \text{ V}$$

Thus, the drain voltage V_1 of Q_2 NMOS transistor is 0.623 V

3. Q for the following circuit , find the labeled node voltages. The NMOS transistors have $V_t = 0.9 \text{ V}$ and $k'_n(W/L) = 1.5 \text{ mA/V}^2$.


3. A

$$\begin{aligned} i_{D1} &= \frac{1}{2} k'_n \left(\frac{W}{L} \right) (v_{GS} - V_t)^2 \\ &= \frac{1}{2} \left(1.5 \times 10^{-3} \frac{\text{A}}{\text{V}^2} \right) [(V_3 - V_4) - 0.9]^2 \\ &= 0.75 (V_3 - V_4 - 0.9)^2 \end{aligned}$$

$$\begin{aligned} i_{D2} &= \frac{1}{2} k'_n \left(\frac{W}{L} \right) (v_{GS} - V_t)^2 \\ &= \frac{1}{2} \left(1.5 \times 10^{-3} \frac{\text{A}}{\text{V}^2} \right) [(V_4 - V_5) - 0.9]^2 \\ &= 0.75 (V_4 - V_3 - 0.9)^2 \end{aligned}$$

$\therefore Q_1$ and Q_2 are in series

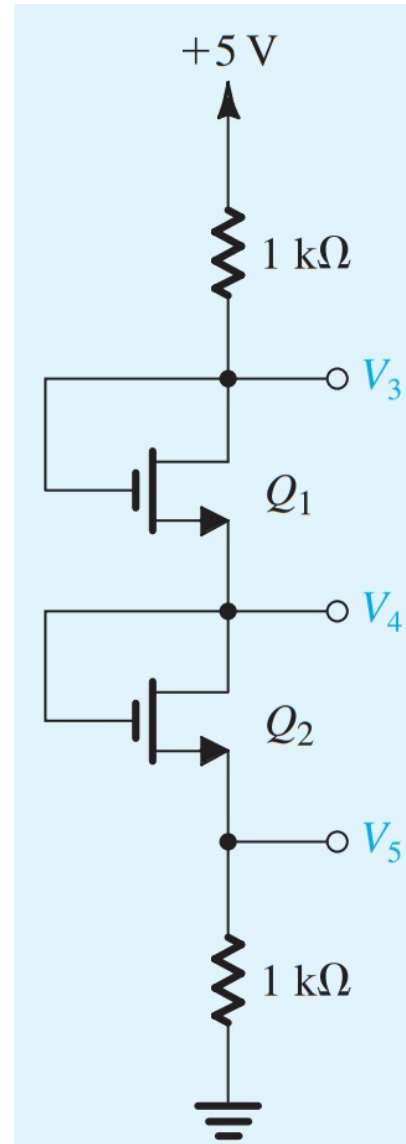\therefore drain current of Q_1 is equal to the drain current of Q_2



$$0.75 (V_3 - V_4 - 0.9)^2 = 0.75 (V_4 - V_5 - 0.9)^2$$

$$\frac{V_3 + V_5}{2} = V_4 \quad (1)$$

For Q_2 transistor :

$$\begin{aligned} i_{D2} &= \frac{V_3 - (0)}{1000} \\ &= V_3 \text{ mA} \end{aligned}$$

$$\begin{aligned} i_{D1} &= \frac{5 - (V_3)}{1000} \\ &= 5 - V_3 \text{ mA} \end{aligned}$$

$$\because i_{D1} = i_{D2}$$

$$\therefore 5 - V_3 = V_3$$

$$V_3 + V_3 = 5$$

Substitute $V_3 + V_5 = 5$ in equation (1)

$$\begin{aligned} V_4 &= \frac{V_3 + V_5}{2} \\ &= \frac{5}{2} = 2.5 \text{ V} \end{aligned}$$

Thus, the drain voltage V_4 of Q_2 NMOS transistor is 2.5 V

$$0.75 (V_3 - V_4 - 0.9)^2 \text{ mA} = V_5 \text{ mA}$$

$$0.75 (V_3 - 2.5 - 0.9)^2 = V_5$$

$$\text{Substitute } V_5 = 0.75 (V_3 - 3.4)^2 \text{ in } V_3 + V_5 = 5 \text{ V}$$

$$V_3 + V_5 = 5 \text{ V}$$

$$V_3 + 0.75 (V_3 - 3.4)^2 = 5$$

$$V_3 + 0.75 (V_3^2 + 11.56 - 6.8V_3) = 5$$

$$0.75V_3^2 - 5.1V_3 + V_3 + 8.67 - 5 = 0$$

$$0.75V_3^2 - 4.1V_3 + 3.67 = 0$$

Solve the equation $0.75V_3^2 - 4.1V_3 + 3.67 = 0$ The drain voltage V_3 of Q_1 NMOS transistor is

$$1.13 \text{ V} \quad \text{or} \quad 4.33 \text{ V}$$

1.13 V is rejected because $V_G > V_S$ for the MOSFET to be $> V_t$.

$$V_3 + V_5 = 5$$

$$V_5 = 5 - V_3$$

$$V_5 = 0.67 \text{ V}$$

Thus, the voltage V_5 is 0.67 V

4. Q In the circuit of the following figure, transistors Q_1 and Q_2 have $V_t = 0.5V$, and the process transconductance parameter $k'_n = 400\mu A/V^2$. Find V_1 , V_2 , and V_3 for each of the following cases:

a) $(W/L)_1 = (W/L)_2 = 10$

b) $(W/L)_1 = 1.5(W/L)_2 = 10$


4. A

a)

Due to the similarity of the circuit :

$$i_{D1} + i_{D2} = 200\mu A$$

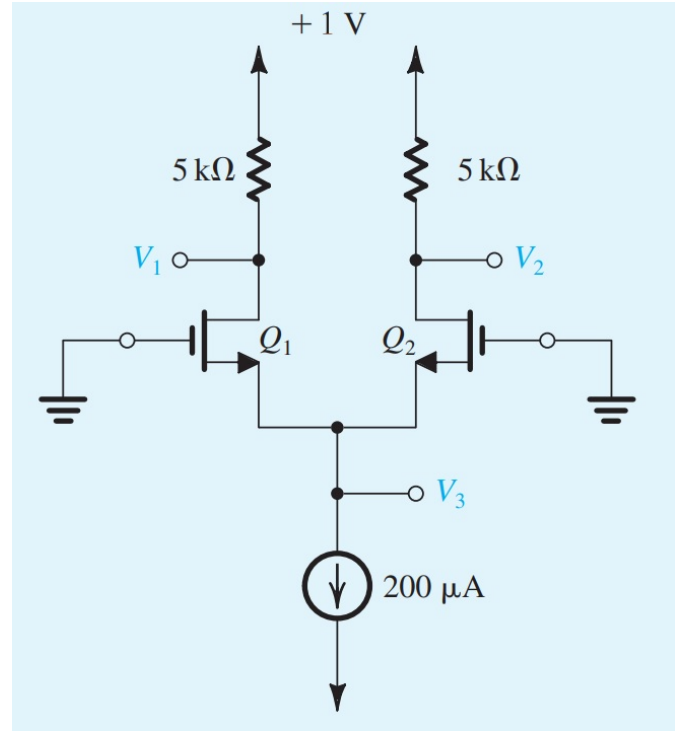Therefore Drain current $i_{D1} = i_{D2}$ is $100\mu A$



$$i_{D1} = \frac{1 - V_1}{5 \times 10^3} \text{ A} \quad (1)$$

$$\begin{aligned} i_{D1} &= \frac{1}{2} k'_n (W/L)_1 (v_G - V_t)^2 \\ &= \frac{1}{2} (400 \times 10^{-6} \text{ A/V}^2) (10) (0 - V_3 - 0.5)^2 \\ &= 2 (V_3 + 0.5)^2 \text{ mA} \end{aligned}$$

substitute with $i_{D1} = 100\mu A$ in (1)

$$100 \times 10^{-6} \text{ A} = \frac{1 - V_1}{5 \times 10^3} \text{ A}$$

$$0.5 = 1 - V_1$$

$$V_1 = 0.5 \text{ V}$$

Drain voltage of Q_1 NMOS transistor V_1 is $0.5V$

Similarly :

Drain voltage of Q_2 NMOS transistor V_2 is $0.5V$

$$i_{D1} = 2 (V_3 + 0.5)^2 \text{ mA}$$

$$100 \times 10^{-6} \text{ A} = 2 (V_3 + 0.5)^2 (10^{-3}) \text{ A}$$

$$(V_3 + 0.5)^2 = 0.05$$

$$V_3 = -0.723 \text{ V}$$

Source voltage V_3 is -0.723 V

$$\text{b) } (W/L)_1 = 10$$

$$(W/L)_2 = 6.66$$

$$\begin{aligned} i_{D1} &= \frac{1}{2} k'_n (W/L)_1 (v_{GS} - V_t)^2 \\ &= \frac{1}{2} (400 \times 10^{-6} \text{ A/V}^2) (10) (0 - V_3 - 0.5)^2 \\ &= 2 (V_3 + 0.5)^2 \text{ mA} \end{aligned}$$

$$\begin{aligned} i_{D2} &= \frac{1}{2} k'_n (W/L)_2 (v_{GS} - V_t)^2 \\ &= \frac{1}{2} (400 \times 10^{-6} \text{ A/V}^2) (6.66) (0 - V_3 - 0.5)^2 \\ &= 1.33 (V_3 + 0.5)^2 \text{ mA} \end{aligned}$$

Divide the two equations :

$$\frac{i_{D1}}{i_{D2}} = \frac{2 (V_3 + 0.5)^2 \text{ mA}}{1.33 (V_3 + 0.5)^2 \text{ mA}}$$

$$\frac{i_{D1}}{i_{D2}} = 1.5$$

Relation between i_{D1} and i_{D2} is $i_{D1} = 1.5i_{D2}$

$$i_{D1} + i_{D2} = 200\mu\text{A}$$

$$1.5i_{D2} + i_{D2} = 200 \times 10^{-6} \text{ A}$$

$$2.5i_{D2} = 200 \times 10^{-6} \text{ A}$$

$$i_{D2} = 80\mu\text{A}$$

Drain current i_{D2} is $80\mu\text{A}$

Therefore Drain current i_{D1} is $120\mu\text{A}$

$$\text{We observed that } i_{D1} = \frac{1 - V_1}{5 \times 10^3} \text{ A}$$

$$i_{D1} = \frac{1 - V_1}{5 \times 10^3} \text{ A}$$

$$120 \times 10^{-6} \text{ A} = \frac{1 - V_1}{5 \times 10^3} \text{ A}$$

$$0.6 = 1 - V_1$$

$$V_1 = 0.4 \text{ V}$$

Drain voltage of Q_2 NMOS transistor V_1 is 0.4V

$$\text{and } i_{D2} = \frac{1 - V_2}{5 \times 10^3} \text{ A}$$

$$i_{D2} = \frac{1 - V_2}{5 \times 10^3} \text{ A}$$

$$80 \times 10^{-6} \text{ A} = \frac{1 - V_2}{5 \times 10^3} \text{ A}$$

$$0.4 = 1 - V_1$$

$$V_2 = 0.6 \text{ V}$$

Drain voltage of Q_1 NMOS transistor V_1 is 0.6V

$$i_{D1} = 2 (V_3 + 0.5)^2 \text{ mA}$$

$$120 \times 10^{-6} \text{ A} = 2 (V_3 + 0.5)^2 (10^{-3}) \text{ A}$$

$$(V_3 + 0.5)^2 = 0.06$$

$$V_3 = -0.744 \text{ V}$$

Source voltage V_3 is -0.744 V